



gradeup

Prep Smart. Score Better.

Computer Organization and Architecture

Logic GATES and Boolean algebra

ABOUT ME : MURALIKRISHNA BUKKASAMUDRAM

- MTech with 20 years of Experience in Teaching GATE and Engineering colleges
- IIT NPTEL Course topper in Theory of computation with 96 %
- IGIP Certified (Certification on International Engineering educator)
- GATE Qualified
- Trained more than 50 Thousand students across the country
- Area of Expertise : TOC,OS,COA,CN,DLD




Logic GATES and Boolean algebra

GATE :- Manipulation of binary information is done by the Logic Circuit is called a GATE

x, y	\downarrow	\downarrow
$x'y'$	0	0
$x'y$	0	1
xy	1	0
xy	1	1

AND

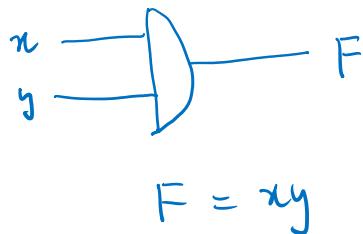

Truth Table

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

OR

$$\begin{aligned}
 F &= x'y + xy' + xy \\
 &= x'y + x(y' + y) \\
 &= x'y + x \\
 &= (x' + x)(y + x) \\
 &= y + x \\
 &= x + y
 \end{aligned}$$

OR



$$F = x + y$$

Truth Table

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1


$$= y + x$$

$$= x + y$$


Logic GATES and Boolean algebra

Not AND

NOT (Inverter)

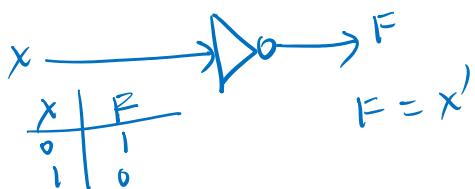

NAND

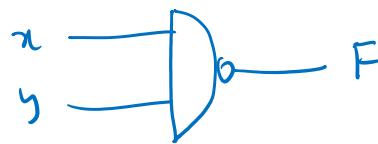

$$F = (xy)'$$

Truth Table

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

$$F = x'y' + xy' + xy$$

$$= x'(y' + y) + xy'$$

$$= x' + xy'$$

$$= (x' + x)(x + y')$$

$$= x' + y'$$

$$= (xy)'$$

NOR [Not OR]



$$F = (x+y)'$$

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0


$$F = x'y'$$

$$F = (x+y)'$$

Logic GATES and Boolean algebra

x	y	F
0	0	0
0	1	1 ✓
1	0	1 ✓
1	1	0


Ex-OR GATE

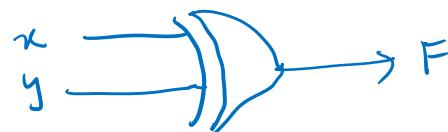

$$F = x'y + xy$$

$$F = x \oplus y$$


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

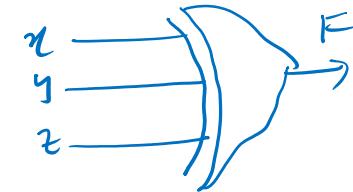

$$F = x \oplus y \oplus z$$

odd function.

Ex-NOR Gate

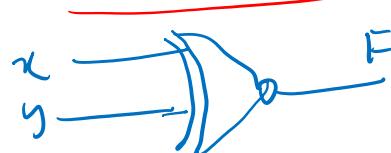

$$F = x \ominus y$$

x	y	F
0	0	1 ✓
0	1	0
1	0	0
1	1	1 ✓

$$F = x'y' + xy = x \ominus y$$

Logic GATES and Boolean algebra

Boolean Algebra

$$\begin{matrix} x \\ 0 \end{matrix} \rightarrow \begin{matrix} 1 \\ 0 \end{matrix}$$

$$\begin{matrix} 0 \\ 1 \end{matrix} \rightarrow \begin{matrix} 0 \\ 1 \end{matrix}$$

$$\begin{matrix} 1 \\ 0 \end{matrix} \rightarrow \begin{matrix} 0 \\ 0 \end{matrix}$$

$$(1) \quad \underline{x \cdot 0 = 0}$$

$$(2) \quad \underline{x \cdot 1 = x}$$

$$(3) \quad \underline{x + 1 = 1}$$

$$(4) \quad \underline{x + 0 = x}$$

$$(5) \quad x + y = y + x$$

$$(6) \quad xy = yx$$

$$(7) \quad (x')' = x$$

$$(8) \quad \underline{(x+y)'} = x'y'$$

$$(9) \quad \underline{(xy)'} = x' + y'$$

$$(10) \quad \underline{x + yz = (x+y)(x+z)}$$

$$(11) \quad \underline{x(yz) = (xy)z}$$

$$(12) \quad \underline{x + (y+z) = (x+y)+z}$$

$$(13) \quad x \cdot x = x$$

$$(14) \quad \underline{x + x = x} \quad 2^n$$

Boolean functions

By using n -boolean variables, we can have 2^{2^n}

boolean functions.

$$\begin{matrix} x & y \\ \uparrow & \uparrow \end{matrix} \quad 2^{2^2} = 16$$

$$x, y, z$$

$$2^{2^3} = 2^8 = 256$$

Logic GATES and Boolean algebra

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	0	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	0	0	1	1	1	0	1	1	1
1	1	0	1	0	1	0	1	0	1	0	0	1	1	0	1	0	1

$$F_0 = 0$$

$$F_1 = xy$$

$$F_2 = xy'$$

$$F_3 = xy' + xy \\ = x(y' + y)$$

$$F_4 = x'y$$

$$F_5 = x'y + xy \\ = (x' + x)y$$

$$F_6 = y$$

$$F_7 = x'y + xy'$$

$$F_8 = x'y' \\ F_9 = (x+y)'$$

$$F_{10} = x'y' + xy' \\ = (x' + x)y'$$

$$F_{11} = x'y' + xy' + xy \\ = x'y' + x(y' + y)$$

$$= x'y' + x = (x' + x)(y' + y) = y + x$$

$$= (x' + x)(y' + y) \\ = (y' + x)$$

$$F_{12} = x'y' + xy \\ = x'(y' + y) \\ = x$$

$$F_{13} = (x+y)'$$

$$F_{14} = x'y' + xy' \\ = (x' + x)y'$$

$$F_{15} = x'y' + xy' + xy \\ = x'y' + x = (x' + x)(y' + y) = y + x$$

Logic GATES and Boolean algebra

$$\begin{aligned}
 F_{13} &= \bar{x}\bar{y} + \bar{x}y + xy \\
 &= \bar{x}\bar{y} + (\bar{x} + x)y \\
 &= \bar{x}\bar{y} + y \\
 &= (\bar{x} + y)(\bar{y} + y) \\
 F_{13} &= \underline{(\bar{x} + y)}
 \end{aligned}$$

$$\begin{aligned}
 F_{14} &= \bar{x}\bar{y} + \bar{x}y + xy \\
 &= \bar{x}(\bar{y} + y) + xy \\
 &= \bar{x} + xy \\
 &= (\bar{x} + x)(\bar{x} + y) \\
 &= (\bar{x} + y) \\
 &= \underline{(xy)'}
 \end{aligned}$$


$$F_{15} = 1$$

Note:— NAND and NOR functions are called Universal building blocks.

Logic GATES and Boolean algebra

OR

$$F = x + y$$

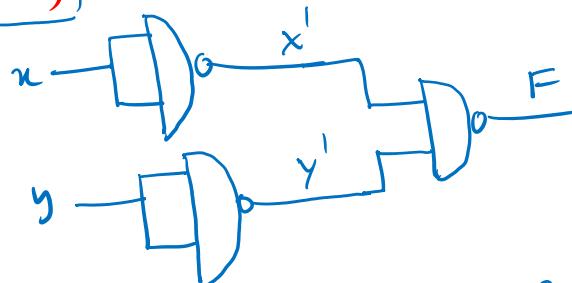

$$F = (x \cdot y)^1 = (x^1)^1 + (y^1)^1$$


$$= x + y$$

\rightarrow OR is realized using NAND Gates.

AND

$$F = xy$$

[AND is realized with NOR Gates]

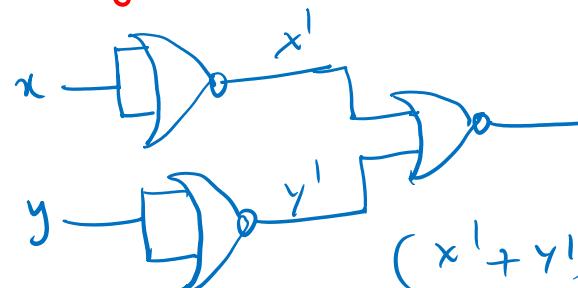

$$(x^1 + y^1)^1 = (x^1)^1 \cdot (y^1)^1$$

$$F = x \cdot y$$

Logic GATES and Boolean algebra

$$0 \rightarrow 1 \\ 1 \rightarrow 0$$

$$\frac{x}{y}$$

Dual Function

$$F = x + y$$

$$F^D = xy$$

OR - AND
AND - OR.

$$\frac{x+0}{x \cdot 1} = \boxed{x'y + y'1}$$

$$(x' + y)(x + y')$$

$$\underline{x'x} + x'y' + yx + \underline{yy'}$$

$$\underline{x'y'} + xy$$

Logic GATES and Boolean algebra

n
 2^{2^n} ✓

Self Dual

$$\underline{F} \quad \underline{F^D}$$

if $F = F^D$ then F is said to be self dual.

$$F = n \quad \checkmark$$

$$F^D = n$$

x, y

$$2^{2^{2-1}} = 4$$

$\binom{n-1}{2^{2^{n-1}}}$ is the total no. of functions which are self dual using n -variables

$$\begin{array}{cccc} x & y & x' & y' \end{array}$$

Logic GATES and Boolean algebra

$$\left(\overline{(P+Q)} + \overline{(Q+R)} \right) + \left(\overline{(P+R)} + \overline{(Q+R)} \right)$$

1. What is the Boolean expression for the output f of the combinational logic circuit of NOR gates given below?

$$(P+Q)' + (Q+R)' \cdot (P+R)' + (Q+R)'$$

$$(P'Q' + Q'R') (P'R' + Q'R')$$

$$P'Q'R' + P'Q'R' + P'Q'R' + Q'R'$$

$$P'Q'R' + Q'R'$$

$$(P'+1)(Q'R')$$


$$Q'R' = \overline{(Q+R)}$$

A. $\overline{Q+R}$


B. $\overline{P+Q}$

C. $\overline{P+R}$

D. $\overline{P+Q+R}$

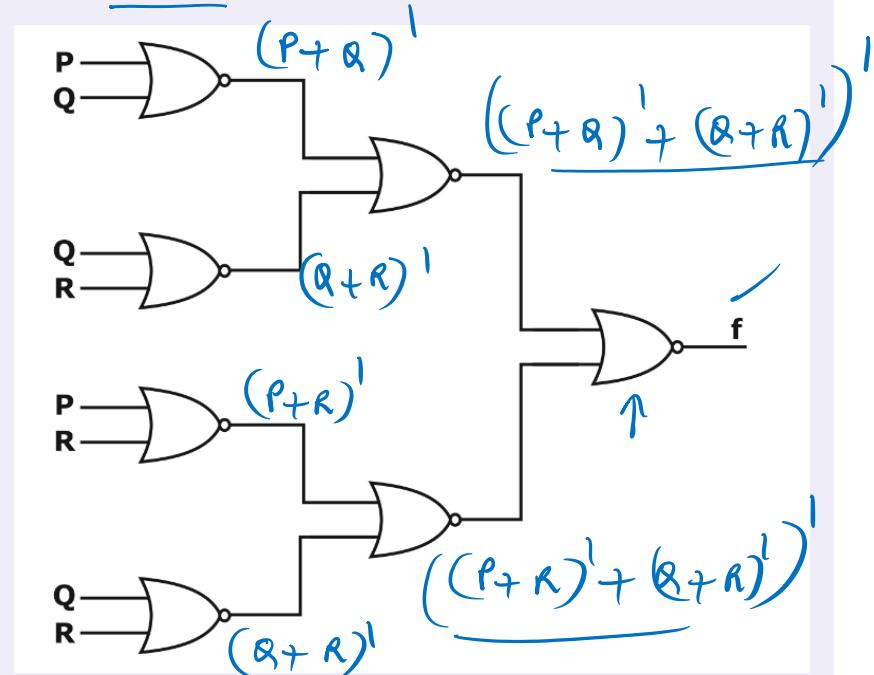

Logic GATES and Boolean algebra

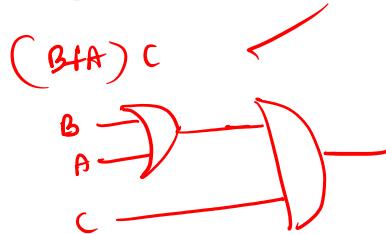

2. Simplify the following expressions using Boolean Algebra

$$(a) \underline{A + AB} = A(1+B) = A \cdot 1 = A$$

$$(b) \underline{AB + AB'} = A(B + 0') = A \cdot 1 = A$$

$$(c) \underline{A'BC + AC} \quad (A'B + A)C = (\underline{A'+A})(B+A) \cdot C = \underline{(0+A)}C$$

$$(d) \underline{A'B + ABC' + ABC} = A'B + AB(C' + C) = A'B + AB$$

$$(e) \underline{AB + A(CD + CD')}$$

$$(f) \underline{(BC' + A'D)(AD' + CD')}$$

$$AB + A [C(D + D')] = AB + A[C]$$

$$\underline{AB + AC}$$

$$\underline{A[B + C]}$$

$$\begin{aligned} & \underline{BC'D} + \underline{BC'CD'} \\ & + \underline{A'DAD'} + \underline{A'DCD'} \\ & \underline{BC'D} \end{aligned}$$

Logic GATES and Boolean algebra

$$xy'z + x'y'z + xyz$$

$$\underline{(x+x')} y'z + xyz$$

$$y'z + xyz$$

$$(y'+xy)z = (y'+x)(\underline{y'+y})z$$

$$(y'+x)z$$

3. Consider Boolean function below

$$F = xy'z + x'y'z + xyz$$

$$\begin{aligned} & AC' + \underline{(A'+A)(A'+B')} C \\ & AC' + A'C + B'C \end{aligned}$$

Simplify the above expression using Boolean Algebra?

$$\begin{aligned} & AC' + \underline{A'C + AB'C} \\ & AC' + \underline{(A'+AB)} C \end{aligned}$$

4. The function $\underline{AB'C + A'BC + ABC' + A'B'C + AB'C'}$ is equivalent to

A. $AC' + AB + A'C$

$$A [BC' + B'C']$$

B. $AB' + AC' + A'C$

$$\underline{A C' [B + B']} = AC'$$

C. $A'B + AC' + AB'$

$$(A'B + A'B') C$$

D. $A'B + AC + AB'$

$$A'C[B + B'] C = A'C$$

Logic GATES and Boolean algebra

$$f(x+y, y) = x'y + y$$

$$(x+y)' + y$$

$$x'y' + y$$

$$(x'+y)(\underline{y'+y})$$

5. Let $f(A, B) = A' + B$. Simplified expression for function

$$\underline{f(f(X+Y, Y), Z)}$$

A. $X' + Z$

B. XYZ

C. $XY' + Z$

D. None

$$\underline{f(A, B) = A' + B}$$


$$\underline{f(f(x+y, y), z)}$$

$$f(\underline{x'+y}, \underline{z})$$

$$(x'+y)' + z$$

$$\underline{x'y' + z}$$

Logic GATES and Boolean algebra

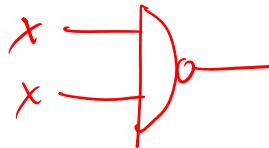

$$(x \cdot x)' = (x)'$$

6. Which of the following expression is not equivalent to \overline{x}

A. $\overline{x \text{ NAND } x}$


B. $\overline{x \text{ NOR } x}$

C. $x \text{ NAND } 1$

D. $\overline{x \text{ NOR } 1} = 0$




$$(x \cdot x)' = \underline{x}'$$

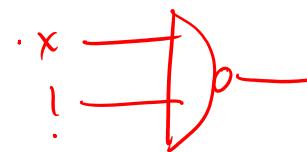

$$x'$$

$$(x \cdot 1)' = x'$$

$$(x \cdot 1)' = \underline{x}'$$

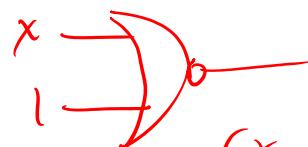

$$(x + 1)'$$

$$(1)' = 0$$


Logic GATES and Boolean algebra

$$((x' + y) \cdot yz)^{'}$$

$$(x' + y)^{'} + (yz)^{'}$$

$$\underline{\underline{xy' + y' + z'}}$$

7. Consider the following circuit

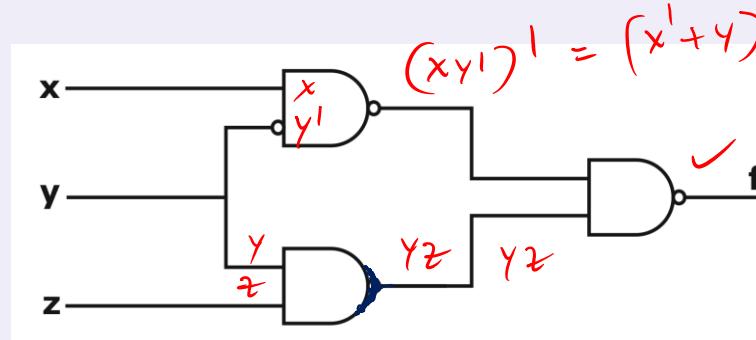

- A. f is Independent of x
- B. f is Independent of y
- C. f is Independent of z
- D. None of These


$$((xy')^{\prime} \cdot (yz))^{'}$$

$$((xy_1)^{'})^{'} + (yz)^{'}$$

$$\underline{\underline{(x+1)y' + z'}}$$


$$xy' + yz'$$

Logic GATES and Boolean algebra

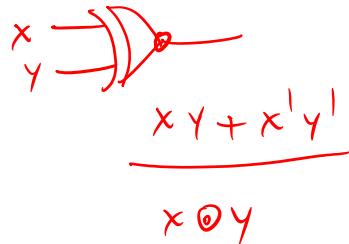


$$x \oplus y = \overline{x'y + x'y'} = x \oplus y$$

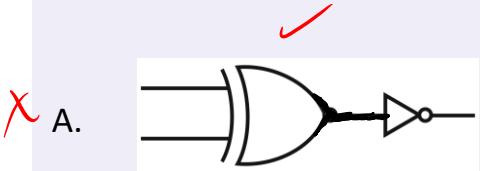
8. Which one of the following circuit is NOT equivalent to a 2-input XNOR gate ?



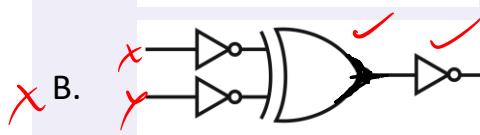
$$(x'y + xy')' = (\overline{x'y})' \cdot (\overline{xy'})' = (x+y) \cdot (x'+y)$$


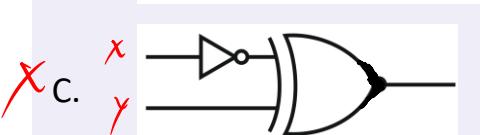
$$(x')'y' + x(y')' = \overline{x'y} + \overline{xy} = \overline{xy} + \overline{x'y}$$


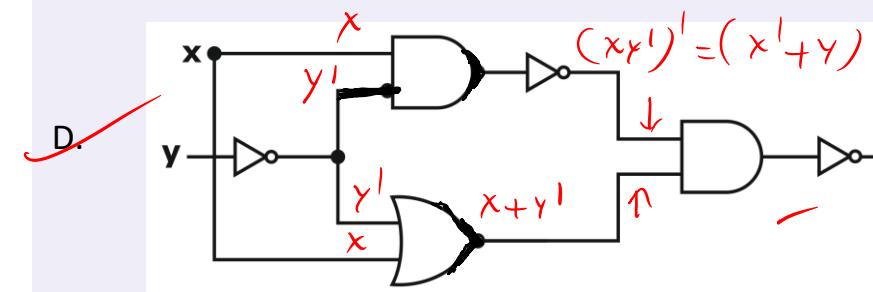
$$(x')'y + x'y' = \overline{x'y} + \overline{xy} = \overline{xy} + \overline{x'y}$$



$$(x'y')' = (x'+y)$$

$$((x'+y)(x+y'))' = (x'+y)' + (x+y')' = \overline{x} \cdot \overline{y} + \overline{x} \cdot y + x \cdot \overline{y} + x \cdot y$$

$$\overline{x} \cdot \overline{y} + \overline{x} \cdot y + x \cdot \overline{y} + x \cdot y$$


Logic GATES and Boolean algebra

$$\begin{array}{c} \overline{(AB+C)} \\ \text{x} \rightarrow \text{o} \quad \text{y} \rightarrow \text{o} \\ F = (x+y)' \end{array}$$

9. What is the minimum number of GATES required to implement the Boolean function $(AB+C)$ if we have to use two input NOR Gates only?

- A. 2
- ~~B. 3~~
- C. 4
- D. 5

$$(AB+C) = \overline{(A+C)(B+C)}$$

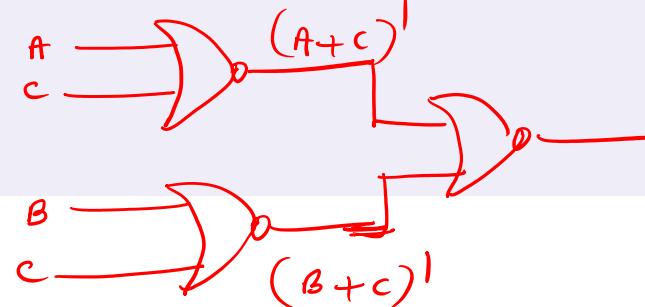

$$\begin{aligned} & ((A+C)' + (B+C)')' \\ &= ((A+C)')' \cdot ((B+C)')' = (A+C)(B+C) \\ & \underline{\underline{AB+BC}} \end{aligned}$$